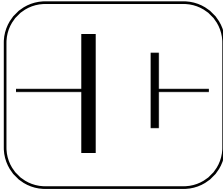



Name: _____ Date: _____




Can you match these circuit symbols to their correct name?




Motor

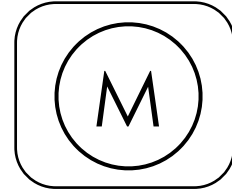


Open switch

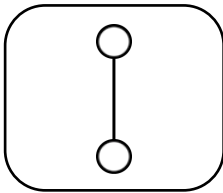


Buzzer

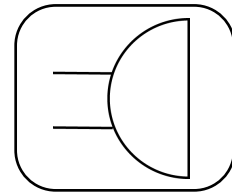

Battery

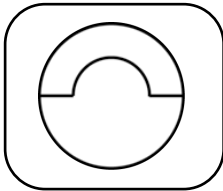

Closed switch

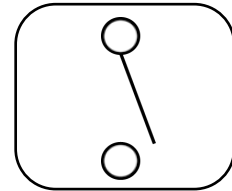

Bulb

Now draw a circuit with these symbols to include a battery, bulb, open switch and wires. Don't forget to use a ruler for the wires!



Blank area for drawing a circuit.