

Name: _____ Date: _____



Can you draw a diagram for each of these circuits using conventional circuit symbols?

Circuit with battery, bulb, open switch, buzzer and wires:

Circuit with two batteries, motor, closed switch and wires:

Circuit with battery, buzzer, open switch, two bulbs and wires:

Circuit with battery, motor, open switch, buzzer and wires: