
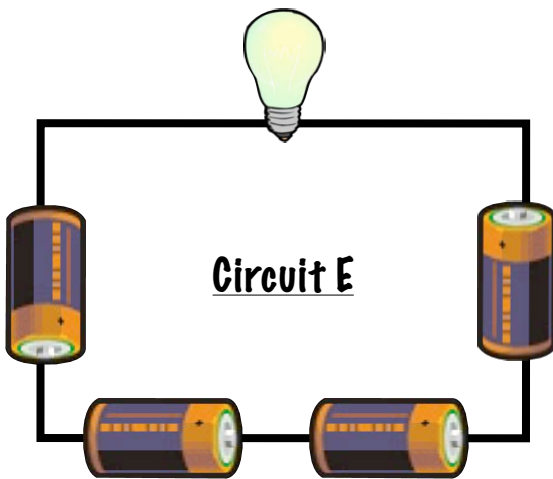
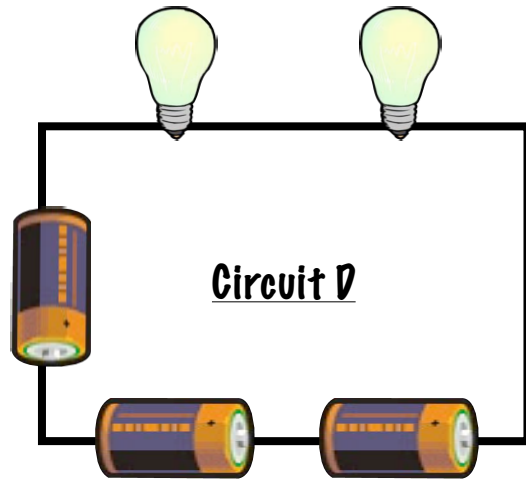
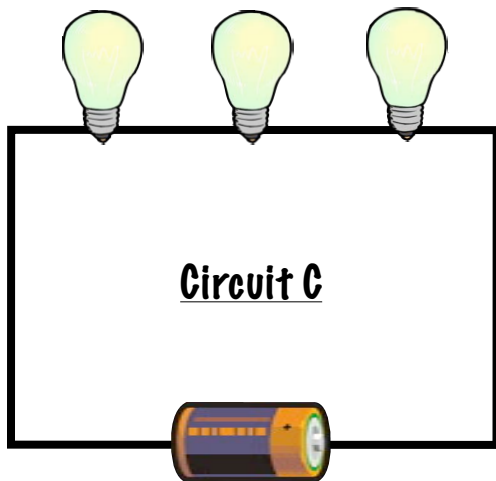
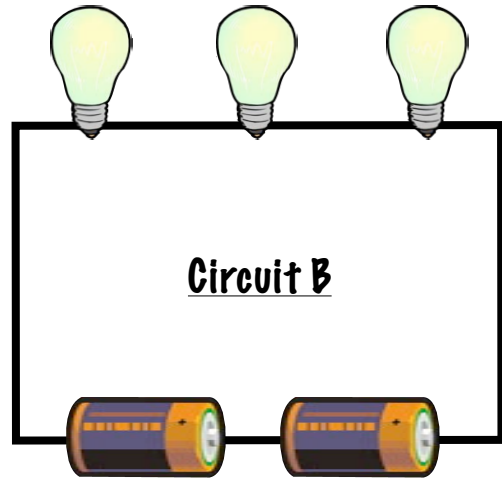


Name: _____ Date: _____

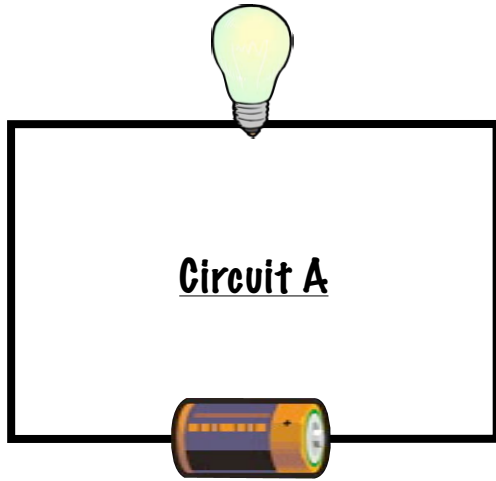Can you order the bulbs in these circuits from the brightest to the dimmest? Each bulb can take 5V and each batteries is 1.5V.



Dullest	
↓	
Brightest	