


Name: _____ Date: _____



Can you use these pictures to help you draw a picture of a working circuit? Make sure everything is linked in the correct places.



bulb

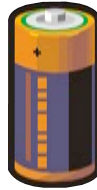

battery



wire

Write TRUE or FALSE in the box next to each statement:

Electrical current needs a complete circuit to flow around or the electrical components (such as light bulbs) will not work.

All materials can conduct electricity. This means wires can be made from any material.

Batteries are the only way of producing electricity.

Batteries, bulbs, motors and buzzers are all electrical components.