

Name: _____ Date: _____



Can you draw a diagram of a series circuit and a parallel circuit in these boxes? Use the words below to label your diagrams:

bulb

switch

wire

battery

Series circuit:

Parallel circuit:

What is the main difference between a series circuit and a parallel circuit?

What kind of circuit would you use for a torch? Why? _____

What kind of circuit would you use for a fairy lights? Why? _____